


# Custom UART(Universal Asynchronous Receiver Transmitter)

By: Ahmed Ebrahim Ahmed Ebrahim

Supervisors: Eng. Mohamed Salah & Eng. Mohamed Tareq

## Project overview:

UART (Universal Asynchronous Receiver-Transmitter) is a widely used protocol for device-to-device serial communication. It enables reliable data transfer with minimal circuitry, typically requiring only two lines (TX and RX) for communication. Its simplicity and cost-effectiveness make it a standard interface in digital systems, embedded processors, and FPGA designs.

 

*Figure 1(UART communication)*

This project presents the design and implementation of a custom UART system in Verilog HDL, supporting both transmission (TX) and reception (RX). The design follows the standard 8 data bits, no parity, 1 stop bit (8N1) frame format, operating at a baud rate of 9600 bps with a 100 MHz system clock. The architecture includes key components such as a Baud Rate Generator, Edge Detector, Frame Generator, FSM Controllers, Bit Selector, MUX, and Serial-to-Parallel Shift Register.

The UART transmitter encapsulates data with start and stop bits and serially outputs each frame using a counter-driven MUX. The receiver detects the start bit via an edge detector, aligns sampling with the baud counter, and reconstructs the parallel data through a shift register under FSM control. Error detection mechanisms validate stop bits and flag invalid frames.

The system was verified using self-checking testbenches in Questa Sim, which applied diverse input patterns and confirmed correct operation through waveform analysis. Results validated accurate frame transmission, reception, and error detection.

This project demonstrates a modular, reusable UART design, showcasing practical skills in RTL design, FSM implementation, simulation, and verification. It provides a solid foundation for

FPGA/ASIC development and can be extended with features such as configurable baud rates, parity support, and FIFO buffering.

## System and specification:

### 1. Protocol Requirements

- **Frame format:** 1 start bit, 8 data bits, no parity, 1 stop bit (8N1).
- **Baud rate:** 9600 bps.
- **System clock:** 100 MHz.
- **Communication type:** Full-duplex (separate TX and RX modules).

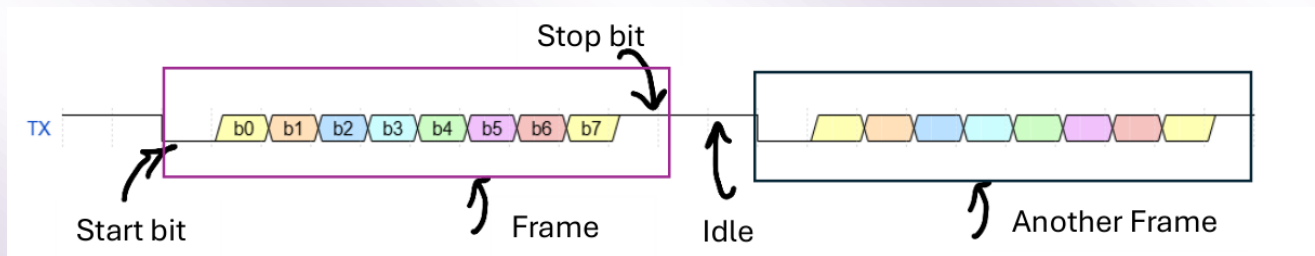


Figure 2(UART Frame Format)

### 2. Functional Requirements

- **Transmitter (UART\_TX):**
  - Accepts 8-bit parallel input.
  - Generates start and stop bits.
  - Outputs serial data stream.
  - Provides status signals (`busy`, `done`).
- **Receiver (UART\_RX):**
  - Detects start bit using edge detector.
  - Samples incoming data at correct baud intervals.
  - Converts serial data to 8-bit parallel output.
  - Validates stop bit; outputs `err` if invalid.
  - Provides status signals (`busy`, `done`).

### 3. Design Constraints

- Operates under a **100 MHz system clock**.
- Fixed **baud rate of 9600 bps** (can be extended later).
- Reset support: asynchronous reset (`arst_n`) and synchronous reset (`rst`).

## 4. I/O Port Definition (Top-Level Modules)

### UART\_TX

| Signal | Direction | Width | Description                       |
|--------|-----------|-------|-----------------------------------|
| Clk    | Input     | 1     | System clock (100 MHz)            |
| rst    | Input     | 1     | Synchronous reset (active high)   |
| arst_n | Input     | 1     | Asynchronous reset (active low)   |
| tx_en  | Input     | 1     | Enable signal for transmission    |
| data   | Input     | 8     | Parallel data input               |
| tx     | Output    | 1     | Serial data output                |
| busy   | Output    | 1     | High when transmission is ongoing |
| Done   | Output    | 1     | High when frame transmission ends |

### UART\_RX


| Signal | Direction | Width | Description                     |
|--------|-----------|-------|---------------------------------|
| Clk    | Input     | 1     | System clock (100 MHz)          |
| rst    | Input     | 1     | Synchronous reset (active high) |
| arst_n | Input     | 1     | Asynchronous reset (active low) |
| rx_en  | Input     | 1     | Enable signal for reception     |

|      |        |   |                                 |
|------|--------|---|---------------------------------|
| rx   | input  | 1 | Serial data input               |
| data | Output | 8 | Parallel data output            |
| busy | Output | 1 | High when reception is ongoing  |
| Done | Output | 1 | High when frame reception ends  |
| err  | Output | 1 | High if stop-bit error detected |


## System Architecture / Design Methodology

### Block Diagram


- UART:**

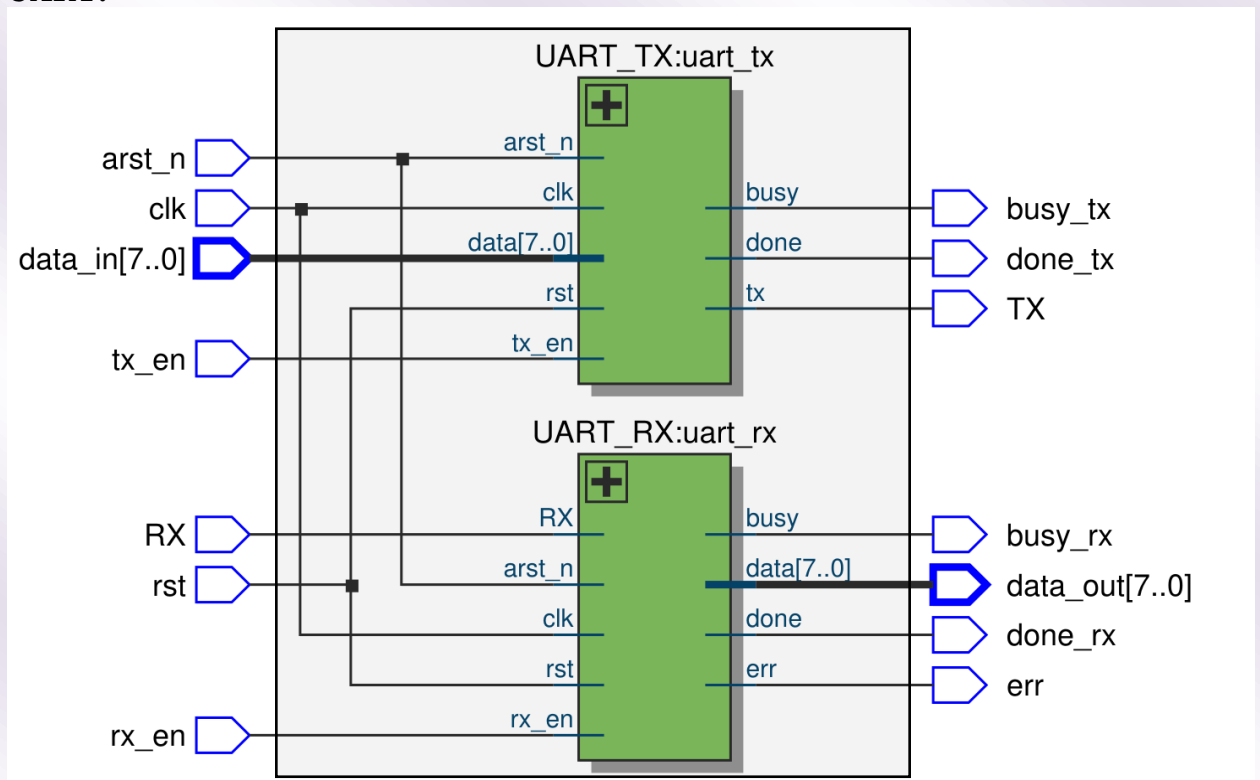

- UART\_TX:**

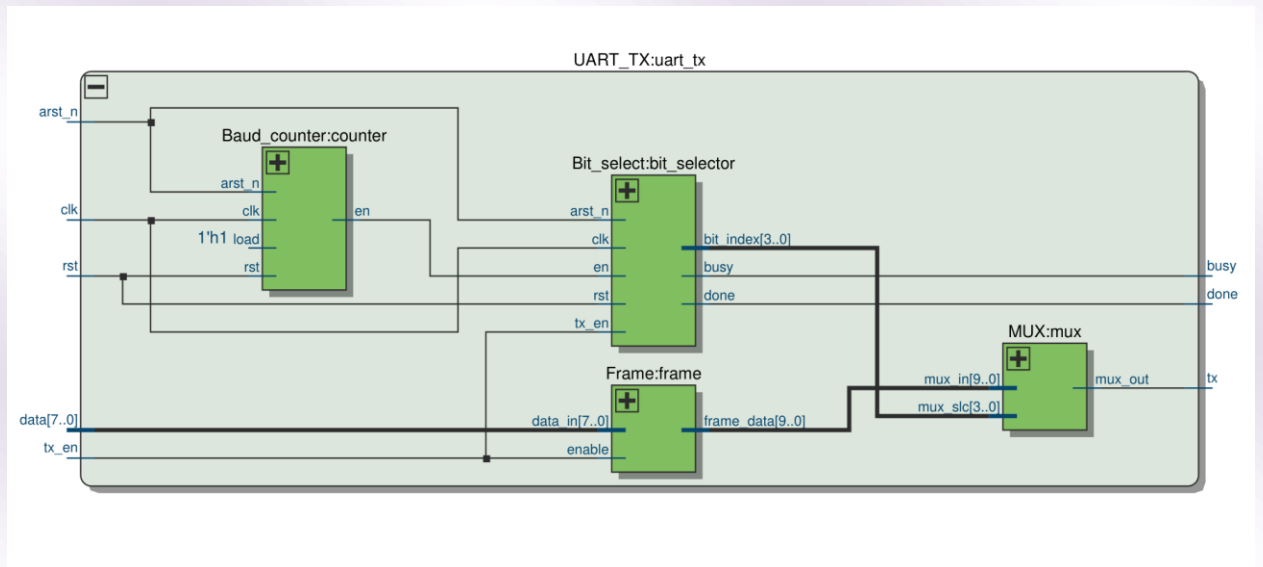

- **UART\_RX:**

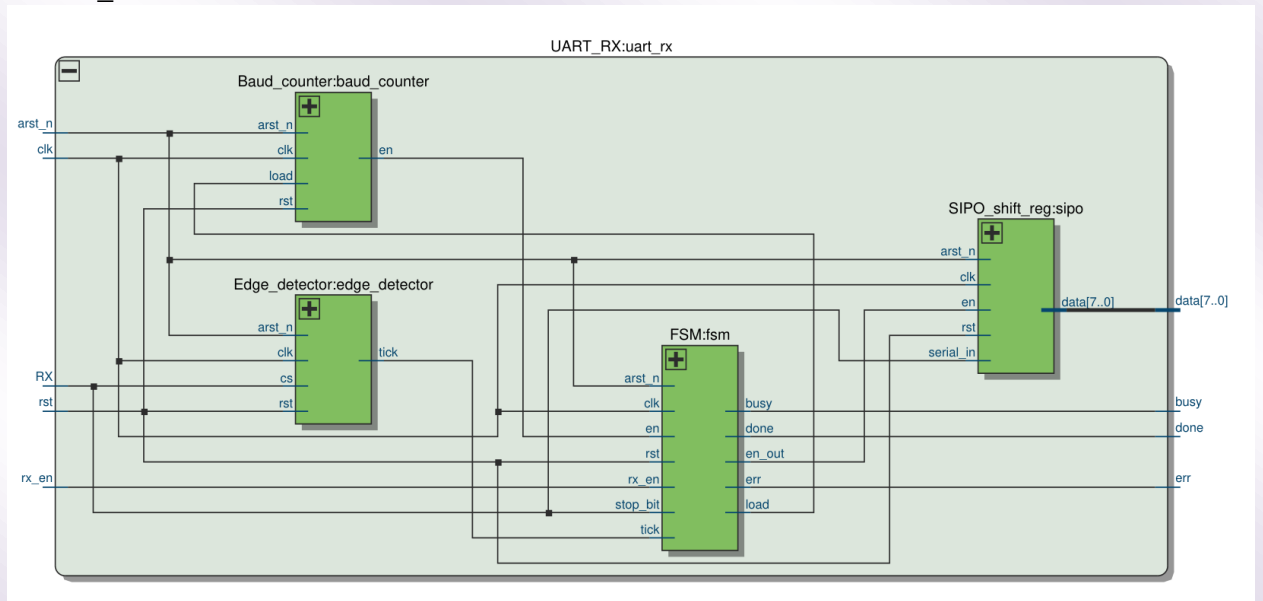

## Modules Description

### Module Name: Baud counter

- **Purpose:** Generates timing signals at the baud rate (9600 bps) from the 100 MHz system clock.
- **Inputs:** `clk`, `rst`, `arst_n`, `load`, `en`.
- **Outputs:** Provides enable pulses for TX and RX modules.

- **Role in System:** Ensures both transmitter and receiver operate synchronously with the correct baud rate.
- **Code:**

```

• module Baud_counter (
•   input load,rst,clk,arst_n,
•   output reg en
• );
•
• reg[13:0] count;
•
• always @(posedge clk or negedge arst_n) begin
•   if (!arst_n) begin
•     count <= load ? 14'd10417 : 14'd5208;
•     en <= 1'b0;
•   end
•   else if (rst) begin
•     count <= load ? 14'd10417 : 14'd5208;
•     en <= 1'b0;
•   end
•   else if (count == 0) begin
•     en <= 1'b1;
•     count <= load ? 14'd10417 : 14'd5208;
•   end
•   else begin
•     en <= 1'b0;
•     count <= count - 1;
•   end
• end
• endmodule

```

#### Module Name: Frame

- **Purpose:** Prepares the parallel data by adding start and stop bits to form the UART frame.
- **Inputs:** data\_in, enable.
- **Outputs:** frame\_data (data + start + stop bits).
- **Role in System:** Converts user input (8-bit data) into a UART frame (10 bits: 1 start, 8 data, 1 stop).
- **Code:**

```

• module Frame #(parameter data_width = 8)(
•   input[data_width-1:0] data_in,
•   input enable,
•   output[data_width+1:0] frame_data

```



```

• );
•
• assign frame_data = enable ? {1'b1, data_in, 1'b0} :
  {(data_width+2){1'b1}};
•
• endmodule
•

```

## Module Name: MUX

- **Purpose:** Selects the correct bit of the UART frame to send out.
- **Inputs:** mux\_in, mux\_slc.
- **Outputs:** mux\_out.
- **Role in System:** Works with the Bit\_select module to output serial data bit by bit during transmission.
- **Code:**

```

• module MUX #(parameter bit_num = 10, parameter slc_num = 3)(
•   input[bit_num-1:0] mux_in,
•   input[slc_num:0] mux_slc,
•   output reg mux_out
• );
•
• always @(*) begin
•   case(mux_slc)
•     4'b0000: mux_out = mux_in[mux_slc];
•     4'b0001: mux_out = mux_in[mux_slc];
•     4'b0010: mux_out = mux_in[mux_slc];
•     4'b0011: mux_out = mux_in[mux_slc];
•     4'b0100: mux_out = mux_in[mux_slc];
•     4'b0101: mux_out = mux_in[mux_slc];
•     4'b0110: mux_out = mux_in[mux_slc];
•     4'b0111: mux_out = mux_in[mux_slc];
•     4'b1000: mux_out = mux_in[mux_slc];
•     4'b1001: mux_out = mux_in[mux_slc];
•     default: mux_out = 1'b1;
•   endcase
• end
• endmodule //MUX
•

```

## Module Name: Bit\_select

- **Purpose:** Controls which bit of the frame is currently being transmitted.
- **Inputs:** clk, rst, arst\_n, en.
- **Outputs:** bit\_index, busy, done.



- **Role in System:** Keeps track of transmission progress and signals when frame transmission is finished.
- Code:

```

• module Bit_select #(parameter bit_num = 10,parameter num_width = 3)(
•   input en,clk,rst,arst_n,tx_en,
•   output reg[num_width:0] bit_index,
•   output reg busy,done
• );
•
• always @(posedge clk or negedge arst_n) begin
•   if (~arst_n) begin
•     bit_index <= {(num_width+1){1'b1}};
•     busy <= 0;
•     done <= 1;
•   end
•   else if (rst) begin
•     bit_index <= {(num_width+1){1'b1}};
•     busy <= 0;
•     done <= 1;
•   end
•   else if (~tx_en) begin
•     bit_index = {(num_width+1){1'b1}};
•   end
•   else begin
•     if (bit_index == {(num_width+1){1'b1}}) begin
•       bit_index <= {(num_width+1){1'b0}};
•     end
•     else begin
•       if (en) begin
•         if (bit_index == bit_num-1) begin
•           busy <= 0;
•           done <= 1;
•           bit_index <= {(num_width+1){1'b0}};
•         end
•         else begin
•           busy <= 1;
•           done <= 0;
•           bit_index <= bit_index + 1;
•         end
•       end
•     end
•   end
• end
• end
• end
• endmodule
•

```

**Module Name:** Edge\_detector

- **Purpose:** Detects the start bit edge on RX line.
- **Inputs:** cs (RX line), clk, rst, arst\_n.
- **Outputs:** tick (indicates a falling edge/start bit detected).
- **Role in System:** Synchronizes receiver with incoming data.
- **Code:**

```
module Edge_detector (  
    input wire cs,clk,rst,arst_n,  
    output reg tick  
);  
  
    reg prev;  
  
    always @(posedge clk or negedge arst_n) begin  
        if (~arst_n) begin  
            prev <= 1'b1;  
            tick <= 1'b0;  
        end  
        else if(rst) begin  
            prev <= 1'b1;  
            tick <= 1'b0;  
        end  
        else begin  
            tick <= prev & ~cs;  
            prev <= cs;  
        end  
    end  
  
endmodule
```

**Module Name:** FSM (Receiver)

- **Purpose:** Controls RX operation using states (Idle, Start, Receive, Stop).
- **Inputs:** clk, rst, tick, rx\_en, stop\_bit.
- **Outputs:** done, err, busy, sample\_en, baud\_load.
- **Role in System:** Manages reception of serial bits, checks stop bit validity, and signals completion/error.
- **Code:**

```
module FSM (  
    input rx_en,tick,stop_bit,en,clk,rst,arst_n,  
    output load,busy,done,err,en_out  
);  
  

```

```

• localparam [2:0]IDEL = 0;
• localparam [2:0]START = 1;
• localparam [2:0]DATA = 2;
• localparam [2:0]STOP = 3;
• localparam [2:0]ERROR = 4;
• localparam [2:0]DONE = 5;
•
• reg[2:0] cs,ns;
• reg[3:0]count;
•
• always @(*) begin
•     if (~rx_en) begin
•         ns = IDEL;
•     end
•     else begin
•         case (cs)
•             IDEL:
•                 if (tick) begin
•                     ns = START;
•                 end
•                 else
•                     ns = IDEL;
•             START:
•                 if (en) begin
•                     ns = DATA;
•                 end
•                 else
•                     ns = IDEL;
•             DATA:
•                 if (en) begin
•                     if (count == 8)
•                         ns = STOP;
•                     else
•                         ns = DATA;
•                 end
•                 else
•                     ns = IDEL;
•             STOP:
•                 if (stop_bit) begin
•                     ns = DONE;
•                 end
•                 else
•                     ns = ERROR;
•             ERROR:
•                 ns = ERROR;
•             DONE:
•                 ns = DONE;
•             default:
•                 ns = IDEL;
•         endcase
•     end
• end

```

```

•     endcase
•     end
• end
•
• always @(posedge clk or negedge arst_n) begin
•     if (~arst_n) begin
•         cs <= IDEL;
•         count <= 0;
•     end
•     else if (rst) begin
•         cs <= IDEL;
•         count <= 0;
•     end
•     else begin
•         cs <= ns;
•         if ((cs == START) && en)
•             count <= 0;
•         else if ((cs == DATA) && en)
•             count <= count + 1;
•     end
• end
•
• assign en_out = ((cs==DATA) && en && (count<8))?1:0;
• assign load = (cs==START)?0:1;
• assign busy = ((cs== START) || (cs==DATA))?1:0;
• assign done = (cs== DONE)?1:0;
• assign err = (cs == ERROR)?1:0;
•
• endmodule //FSM
•

```

**Module Name:** SIPO\_shift\_reg

- **Purpose:** Converts received serial bits into parallel data.
- **Inputs:** clk, rst, serial\_in, en.
- **Outputs:** data (8-bit parallel output).
- **Role in System:** Builds the received byte from serial input.
- **Code:**

```

• module SIPO_shift_reg (
•     input serial_in,en,clk,rst,arst_n,
•     output reg[7:0] data
• );
•
• always @(posedge clk or negedge arst_n) begin
•     if (~arst_n) begin

```

```

•     data <= {8{1'b0}};
•     end
•     else if(rst) begin
•         data <= {8{1'b0}};
•     end
•     else if (en) begin
•         data <= {serial_in,data[7:1]};
•     end
• end
•
• endmodule //SIPO_shift_reg
•

```

### Module Name: UART\_TX

- **Purpose:** Handles transmission of data.
- **Submodules:** Frame, Baud\_counter, Bit\_select, MUX.
- **Role in System:** Takes parallel data, frames it, and shifts out serially at the correct baud rate.
- **Code:**

```

• module UART_TX #(parameter data_width = 8)(
•     input tx_en,rst,arst_n,clk,
•     input[data_width-1:0] data,
•     output done,busy,tx
• );
• localparam tx_load = 1;
• wire[data_width+1:0] frame_data;
• wire en;
• wire[3:0] mux_slc;
•
• Baud_counter
counter(.rst(rst),.clk(clk),.arst_n(arst_n),.en(en),.load(tx_load));
• Frame
#(data_width)frame(.data_in(data),.enable(tx_en),.frame_data(frame_data));
• Bit_select #(10,3)
bit_selector(.en(en),.clk(clk),.rst(rst),.arst_n(arst_n),.bit_index(mux_slc),.busy(busy),.done(done),.tx_en(tx_en));
• MUX #(10,3)mux(.mux_in(frame_data),.mux_slc(mux_slc),.mux_out(tx));
•
• endmodule //UART_TX
•

```

### Module Name: UART\_RX

- **Purpose:** Handles reception of data.
- **Submodules:** Edge\_detector, FSM, Baud\_counter, SIPO\_shift\_reg.
- **Role in System:** Detects start bit, samples incoming bits, and outputs received byte with error detection.
- **Code:**

```

• module UART_RX (
•   input  RX,rx_en,clk,rst,arst_n,
•   output done,err,busy,
•   output [7:0] data
• );
•
•   wire baud_load,sample_en,tick,baud_en;
•
•   Edge_detector edge_detector(
•     .clk(clk),
•     .rst(rst),
•     .arst_n(arst_n),
•     .cs(RX),
•     .tick(tick)
•   );
•   FSM fsm(
•     .clk(clk),
•     .rst(rst),
•     .arst_n(arst_n),
•     .done(done),
•     .err(err),
•     .busy(busy),
•     .tick(tick),
•     .stop_bit(RX),
•     .rx_en(rx_en),
•     .en(baud_en),
•     .load(baud_load)
•     ,.en_out(sample_en)
•   );
•   SIPO_shift_reg sipo(
•     .clk(clk),
•     .rst(rst),
•     .arst_n(arst_n),
•     .serial_in(RX),
•     .data(data),
•     .en(sample_en)
•   );
•   Baud_counter baud_counter(
•     .clk(clk),
•     .rst(rst),

```

```

•   .arst_n(arst_n),
•   .load(baud_load),
•   .en(baud_en)
•   );
•
•   endmodule
•

```

**Module Name:** UART (Top-Level)

### Inputs

- **RX** : Serial input data line from external device.
- **clk** : System clock (100 MHz).
- **rst** : Synchronous reset.
- **arst\_n** : Asynchronous active-low reset.
- **rx\_en** : Enable signal for the receiver.
- **tx\_en** : Enable signal for the transmitter.
- **data\_in[7:0]** : 8-bit parallel data to be transmitted.

### Outputs

- **data\_out[7:0]** : 8-bit parallel data received.
- **TX** : Serial output data line to external device.
- **err** : Error flag (framing or invalid data in RX).
- **done\_rx** : High when receiver successfully receives a frame.
- **busy\_rx** : Indicates receiver is currently processing data.
- **done\_tx** : High when transmission of data is completed.
- **busy\_tx** : Indicates transmitter is currently busy.

### Function

The **UART** module acts as the **top-level wrapper** for the UART system. It integrates the transmitter (**UART\_TX**) and receiver (**UART\_RX**) modules, providing a unified interface for bidirectional serial communication. Based on enable signals (**tx\_en** / **rx\_en**), the module handles both sending and receiving operations simultaneously, ensuring proper synchronization with system resets.

### Role in System

This module represents the **user-facing interface** of the UART design. It abstracts the internal details of transmission and reception, exposing only necessary control, status, and data signals. It enables the system to interact with external devices via the UART protocol in a simple plug-and-play fashion.




## Design Methodology

The design of the custom UART follows a structured, modular approach to ensure clarity, reusability, and correctness. The main design principles adopted are:
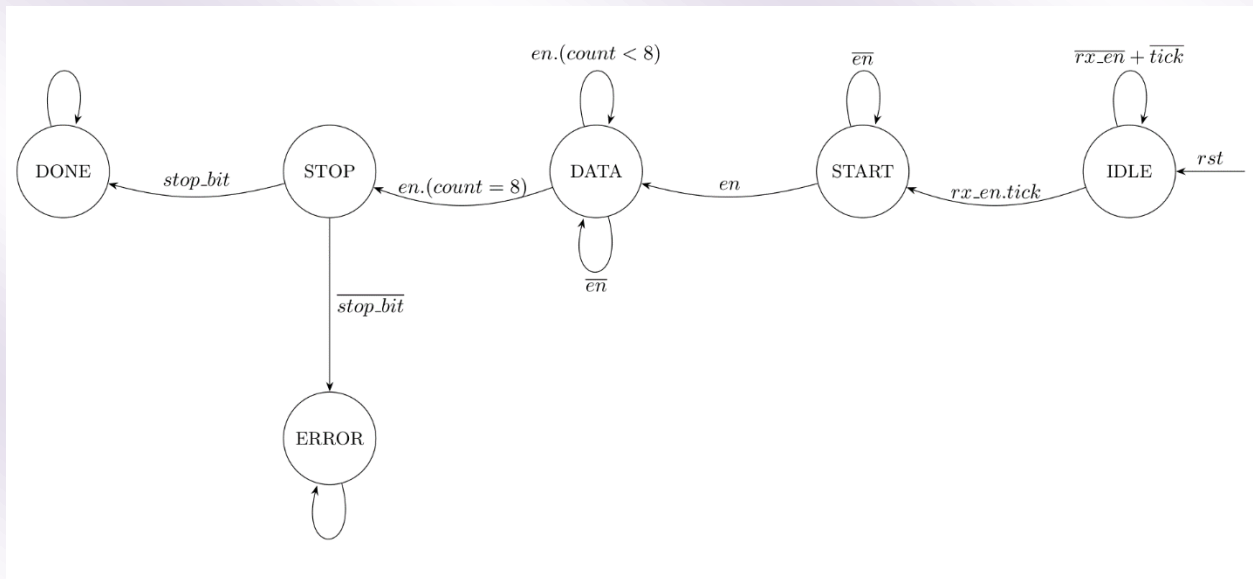
### 1. FSM-Based Design

- The **RX module** relies on a finite state machine with clearly defined states (IDLE, START, DATA, STOP, DONE, ERROR). This ensures predictable behavior, error detection, and synchronization with the baud tick.
- **Diagram:**



### 2. Clock Domain Synchronization

- The UART operates from a **100 MHz system clock**, while communication timing is derived from a **baud rate generator** that provides baud ticks (9600 bps).
- This ensures accurate sampling of received bits and correct timing for transmitted frames.
- Care was taken to synchronize control signals crossing between the system clock and baud tick domains to avoid metastability.

### 3. Reset Strategy

- Both **asynchronous reset** (`arst_n`) and **synchronous reset** (`rst`) are supported.
- Asynchronous reset guarantees a safe start-up condition immediately after power-on.
- Synchronous reset ensures controlled initialization during simulation and runtime, improving reliability in FPGA implementation.

### 4. Simulation-Driven Verification

- Each module (Baud Counter, FSMs, SIPO, Bit Select, TX/RX) was individually verified through **Questa Sim simulation**.

- Testbenches were written to validate correct data transmission, reception, error detection and transmission enabling.

## Testbenches:

### Transmitting Data test:

Code:

```
module TX_tb ();

reg tx_en,rst,arst_n,clk;
reg[7:0] data;
reg [9:0] exp_tx,tx_word;
wire done,busy,tx;

UART_TX
uart_tx(.tx_en(tx_en),.rst(rst),.arst_n(arst_n),.clk(clk),.data(data),
),.done(done),.busy(busy),.tx(tx));

initial begin
    clk = 0;
    forever begin
        #5 clk = ~clk;
    end
end

integer i;

initial begin
    testing(8'b11110000);
    testing(8'b00001111);
    testing(8'b10101010);
    testing(8'b01010101);
    testing(8'b00000000);
    testing(8'b11111111);
    testing(8'b11000001);
    testing(8'b01110100);
    testing(8'b01110010);

    $stop;
end

task testing(input [7:0]data_in);begin
    rst = 1;
```


```

arst_n = 0;
tx_en = 0;
#5
tx_word = {10{1'b0}};
rst = 0;
arst_n = 1;
data = data_in;
exp_tx = {1'b1,data_in,1'b0};
tx_en = 1;
for (i = 0 ; i < 10;i = i+1 ) begin
    #104170
    tx_word[i] = tx;
end
if (exp_tx != tx_word) begin
    $display("Error!");
    $stop;
end
else
    $display("based!");
#104170;
end
endtask

endmodule //TX_tb

```

**Wave form:**

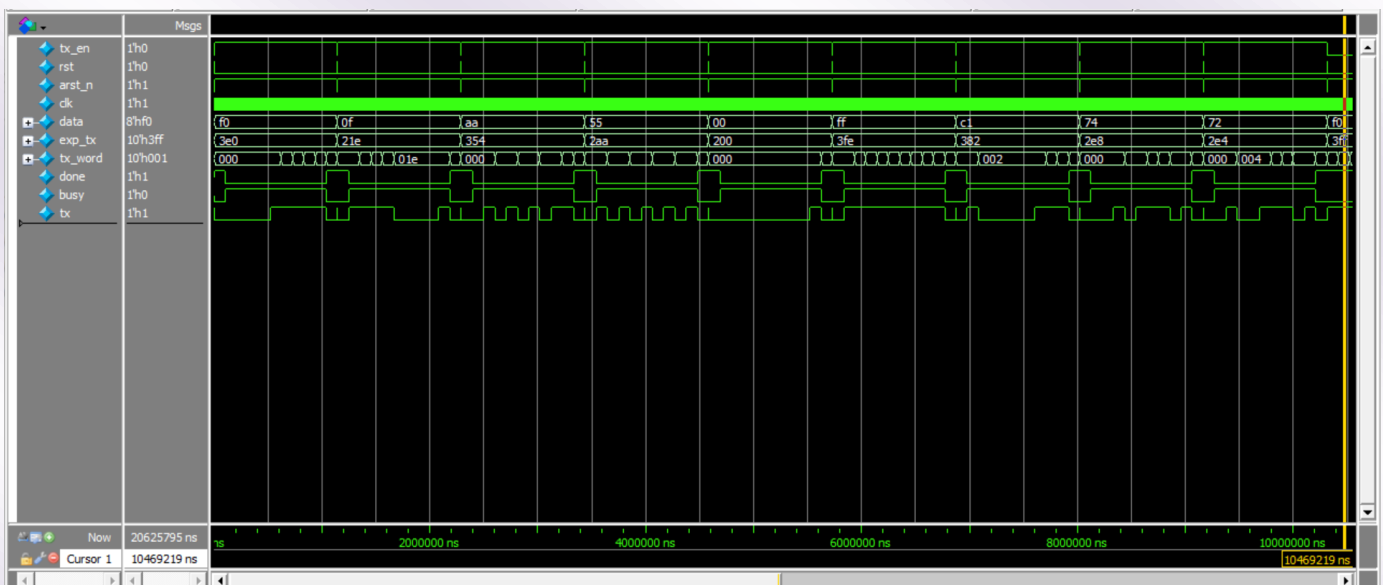

## TX enable test:

### Code:

```
module TX_tb ();

reg tx_en,rst,arst_n,clk;
reg[7:0] data;
reg [9:0] exp_tx,tx_word;
wire done,busy,tx;

UART_TX
uart_tx(.tx_en(tx_en),.rst(rst),.arst_n(arst_n),.clk(clk),.data(data)
),.done(done),.busy(busy),.tx(tx));

initial begin
    clk = 0;
    forever begin
        #5 clk = ~clk;
    end
end

integer i;

initial begin

    testing_en(8'b11110000);
    testing_en(8'b00001111);
    testing_en(8'b10101010);
    testing_en(8'b01010101);
    testing_en(8'b00000000);
    testing_en(8'b11111111);
    testing_en(8'b11000001);
    testing_en(8'b01110100);
    testing_en(8'b01110010);
    $stop;
end


task testing_en(input [7:0]data_in);begin
    rst = 1;
    arst_n = 0;
    tx_en = 0;
```

```

#5
tx_word = {10{1'b0}};
rst = 0;
arst_n = 1;
#5
data = data_in;
exp_tx = {10{1'b1}};
for (i = 0 ; i < 10;i = i+1 ) begin
    #104170
    tx_word[i] = tx;
end
if (exp_tx != tx_word) begin
    $display("Error!");
    $stop;
end
else
    $display("based!");
#104170;
end
endtask
endmodule //TX_tb

```

Wave form:

 

## Receiving Data test:

Code:

```
module RX_tb ();

reg RX,rx_en,clk,rst,arst_n;
wire done_rx,err,busy;
wire [7:0]data_rx;
reg[9:0] tx_word;

UART_RX uart_rx(
    .RX(RX),
    .rx_en(rx_en),
    .clk(clk),
    .rst(rst),
    .arst_n(arst_n),
    .done(done_rx),
    .err(err),
    .busy(busy),
    .data(data_rx)
);

initial begin
    clk = 0;
    forever begin
        #5 clk = ~clk;
    end
end

integer i;

initial begin
    testing(8'b01010101);
    testing(8'b10101010);
    testing(8'b11111111);
    testing(8'b00000000);
    testing(8'b11110000);
    testing(8'b00001111);
    testing(8'b10110100);
    testing(8'b01101101);
    $stop;
end
```

```

task testing(input [7:0] data_in);begin
    RX = 1;
    tx_word = {1'b1,data_in,1'b0};
    rst = 1;
    arst_n = 0;
    rx_en = 0;
    RX = 1;
    #10
    rst = 0;
    arst_n = 1;
    rx_en = 1;
    #50
    for (i = 0 ; i < 10;i = i+1 ) begin
        #104170
        RX = tx_word[i];
    end
    #104170
    if (data_in!=data_rx) begin
        $display("Error detected!");
        $stop;
    end
    else
        $display("Test based!");


    #104170;
end
endtask

endmodule

```



## Wave form:

 

## Error detection test:

### Code:

```
module RX_tb ();

reg RX,rx_en,clk,rst,arst_n;
wire done_rx,err,busy;
wire [7:0]data_rx;
reg[9:0] tx_word;

UART_RX uart_rx(
    .RX(RX),
    .rx_en(rx_en),
    .clk(clk),
    .rst(rst),
    .arst_n(arst_n),
    .done(done_rx),
    .err(err),
    .busy(busy),
    .data(data_rx)
);
```

```

initial begin
    clk = 0;
    forever begin
        #5 clk = ~clk;
    end
end

integer i;


initial begin
    error_test(8'b01010101);
    error_test(8'b10101010);
    error_test(8'b11111111);
    error_test(8'b00000000);
    error_test(8'b11110000);
    error_test(8'b00001111);
    error_test(8'b10110100);
    error_test(8'b01101101);
    $stop;
end

task error_test(input [7:0] data_in);begin

    RX = 1;
    tx_word = {1'b0,data_in,1'b0};
    rst = 1;
    arst_n = 0;
    rx_en = 0;
    RX = 1;
    #10
    rst = 0;
    arst_n = 1;
    rx_en = 1;
    #50
    for (i = 0 ; i < 10;i = i+1 ) begin
        #104170
        RX = tx_word[i];
    end
    #104170;
end
endtask
endmodule

```

## Wave form:

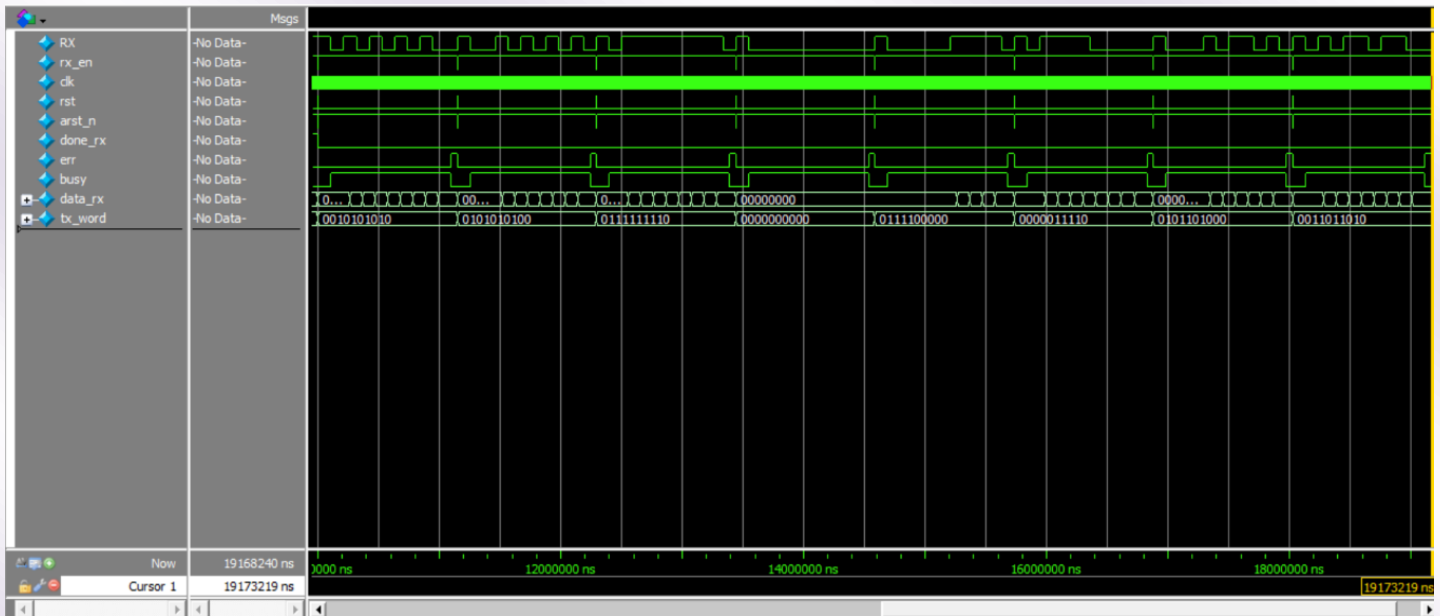

## Conclusion

This project successfully demonstrated the design and implementation of a UART (Universal Asynchronous Receiver-Transmitter) using Verilog HDL. The system was structured into modular components including the transmitter, receiver, baud rate generator, frame generator, FSM controller, and supporting logic, ensuring clarity and scalability of the design.

Simulation results verified correct data transmission and reception under the 8N1 format (8 data bits, no parity, 1 stop bit) at a baud rate of 9600 bps with a 100 MHz system clock. The RX and TX testbenches confirmed reliable operation by testing multiple data patterns and validating correct frame generation, synchronization, and error detection.

Beyond achieving the functional goals, this work provided valuable hands-on experience with FSM-based design, RTL coding, and verification methodologies. It also emphasized the importance of modularity, reset strategies, and simulation-driven validation in digital system design.

The developed UART can serve as a foundation for more advanced communication modules, and can be further extended with features such as configurable baud rates, parity bit options, FIFO buffering, and FPGA-based hardware testing for real-world applications.